

MT02, prob 1

$$a = \frac{qE}{m} = \frac{1.6 \times 10^{-19} \times 620}{1.67 \times 10^{-27}} = 5.94 \times 10^{10} \frac{m}{s^2}$$

$$\Delta x = \frac{V_f^2 - V_i^2}{2a} = \frac{(1.40 \times 10^6)^2 - 0^2}{2 \times (5.94 \times 10^{10})} = 16.5 \text{ m}$$

MT02, prob 2



$$V = \frac{kq}{r} = - \frac{8.99 \times 10^9 \times 1.6 \times 10^{-19}}{(3.00 \times 10^3)} = -4.80 \times 10^{-7} \text{ V}$$

MT02, prob 3

$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{C} + \dots + \frac{1}{C} = \frac{100}{C}$$

$$\Rightarrow C_{eq} = \frac{C}{100}$$

MT02, prob 4

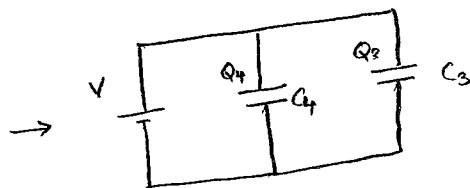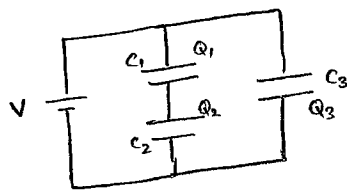

$$\frac{1}{C_4} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{10} + \frac{1}{20} = \frac{3}{20} \Rightarrow C_4 = \frac{20}{3} \mu F$$

$$Q_4 = VC_4 = 10 \text{ V} \times \frac{20}{3} \mu F = \frac{200}{3} \mu C$$

$$Q_1 = Q_4 = \frac{200}{3} \mu C = 66.7 \mu C$$

MT02, prob 5

$$\text{Energy} \times 0.10 \frac{\text{USD}}{\text{kWh}} = 50 \text{ USD.}$$

$$1 \text{ kWh} = 10^3 \times 3600 \text{ J} \\ = 3.6 \times 10^6 \text{ J}$$

$$\text{Energy} = \frac{50}{0.10} \times 3.6 \times 10^6 \text{ J} \\ = 1.8 \times 10^9 \text{ J}$$

MT02, prob 6

$$R = \frac{V}{I} = \frac{\rho l}{A}$$

$$\rho = \frac{VA}{Il} = \frac{2.0 \times (2 \times 10^{-6})}{3.7 \times 1.9} = 5.69 \times 10^{-7} \Omega \text{m.}$$

MT02, prob 7

$$P = IV = \frac{Q}{t} V$$

$$Q = \frac{Pt}{V} = \frac{60 \times (12 \times 60 \times 60)}{120} = 21600 \text{ C} = 2.16 \times 10^4 \text{ C.}$$

MT02, prob 8

$$(a) \quad \frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \Rightarrow R_{eq} = \frac{R}{3} = 100.0 \Omega$$


$$(b) \quad V = 10 \text{ V} \quad \text{for all three resistors}$$

$$(c) \quad I_{eq} = \frac{V}{R_{eq}} = \frac{10.0}{100.0} = 0.100 \text{ A}$$

$$I = \frac{I_{eq}}{3} = 0.033 \text{ A} = 33 \text{ mA} \quad \rightarrow \text{same for each resistor}$$

$$(d) \quad P = IV = 33 \text{ mA} \times 10 \text{ V} \\ = 0.33 \text{ W} \quad \rightarrow \text{same for each resistor.}$$

MT02, prob 9

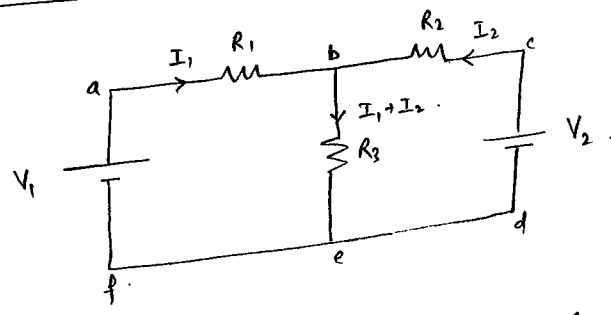

$$V_1 - I_1 R_1 - (I_1 + I_2) R_3 = 0 \Rightarrow (R_1 + R_3) I_1 + R_3 I_2 = V_1$$


$$V_2 - I_2 R_2 - (I_1 + I_2) R_3 = 0 \Rightarrow R_3 I_1 + (R_2 + R_3) I_2 = V_2$$

$$I_1 = \frac{V_1 (R_2 + R_3) - V_2 R_3}{(R_1 + R_3)(R_2 + R_3) - R_3^2} = \frac{V_1 R_2 + (V_1 - V_2) R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$I_1 = 0 \Rightarrow V_1 R_2 + (V_1 - V_2) R_3 = 0$$

$$R_3 = \frac{V_1}{V_2 - V_1} R_2 = \frac{10}{20 - 10} \times 20 \Omega = 20 \Omega$$

MT02, prob 10

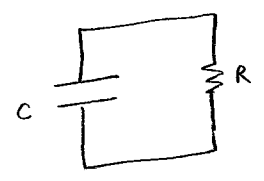

$$Q(t) = Q_0 e^{-\frac{t}{RC}}$$

$$\tau = RC$$

Given $Q(t) = Q_0 - \frac{2}{3} Q_0$

$$= \frac{1}{3} Q_0$$

$$\frac{1}{3} Q_0 = Q_0 e^{-\frac{t}{\tau}}$$

$$\ln \frac{1}{3} = -\frac{t}{\tau}$$

$$t = \tau \ln 3$$