

# Solutions


(MT-02, PHYS-205B, 2015 Fall)

Prob. 1

$$V = \frac{kQ_1}{d/2} + \frac{kQ_2}{d/2}$$

$$= + \frac{9.0 \times 10^9 \times 4.0 \times 10^{-9}}{(1\text{m}/2)} - \frac{9.0 \times 10^9 \times 2.0 \times 10^{-9}}{(1\text{m}/2)}$$

$$= +72 - 36 = 36 \text{ Volt}$$

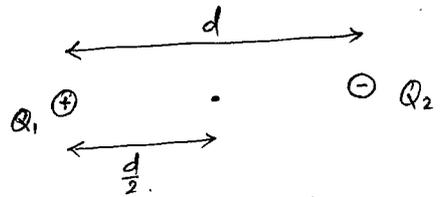


Prob. 2

$$U_i = \frac{kq^2}{L} + \frac{kq^2}{L} + \frac{kq^2}{\sqrt{2}L} = \left(2 + \frac{1}{\sqrt{2}}\right) \frac{kq^2}{L}$$

$$U_f = U_i + \frac{kq^2}{L} + \frac{kq^2}{L} + \frac{kq^2}{\sqrt{2}L} = 2U_i$$

$$U_f - U_i = U_i = \left(2 + \frac{1}{\sqrt{2}}\right) \frac{kq^2}{L}$$

$$= \left(2 + \frac{1}{\sqrt{2}}\right) \frac{8.99 \times 10^9 \times (1.00 \times 10^{-6})^2}{(0.100 \text{ m})} = 0.243 \text{ Joules.}$$

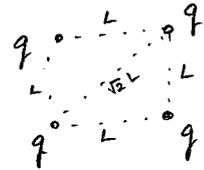

Prob. 3

$$E_x = -\frac{\partial V}{\partial x} = -b$$

$$E_y = -\frac{\partial V}{\partial y} = 0$$

$$E_z = -\frac{\partial V}{\partial z} = 0$$

$$\vec{E} = -b \hat{i}$$

$$= +450 \hat{i} \frac{\text{V}}{\text{cm}}$$

$$= \hat{i} 4.5 \times 10^4 \frac{\text{V}}{\text{m}}$$

Prob. 4

Electric field is zero inside the conductor.

Electric potential is uniform inside a conductor.


$$E = 0$$

$$V = \frac{kQ}{R} = \frac{9.0 \times 10^9 \times 1.0 \times 10^{-6}}{0.10 \text{ m}} = 9.0 \times 10^4 \text{ V}$$

Prob. 5

$$\frac{1}{2} m_2 v_{2i}^2 + \frac{k q_1 q_2}{r_i} = \frac{1}{2} m_2 v_{2f}^2 + \frac{k q_1 q_2}{r_f}$$

$\downarrow = 0$

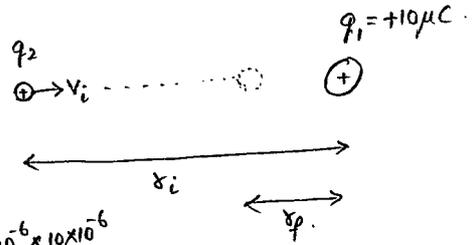

$$\frac{1}{2} 10^{-2} 10^2 + \frac{9.0 \times 10^9 \times 1.0 \times 10^{-6} \times 10 \times 10^{-6}}{0.30} = \frac{9.0 \times 10^9 \times 1.0 \times 10^{-6} \times 10 \times 10^{-6}}{r_f}$$

$$0.5 + 0.30 = \frac{0.090}{r_f} \Rightarrow r_f = 0.11 \text{ m} = 11 \text{ cm}$$

Prob. 6

(a)  $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{10} + \frac{1}{20} = \frac{3}{20} \Rightarrow C_{eq} = 6.7 \mu\text{F}$

(b)  $Q_1 = Q_2 = C_{eq} V = 6.7 \mu\text{F} \times 10 \text{ V} = 67 \mu\text{C}$

(c)  $V_1 = \frac{Q_1}{C_1} = \frac{67 \mu\text{C}}{10 \mu\text{F}} = 6.7 \text{ V}$

$V_2 = \frac{Q_2}{C_2} = \frac{67 \mu\text{C}}{20 \mu\text{F}} = 3.3 \text{ V}$

(d)  $U_1 = \frac{Q_1^2}{2C_1} = \frac{(67 \mu\text{C})^2}{2 \times 10 \mu\text{F}} = 224 \mu\text{J}$

$U_2 = \frac{Q_2^2}{2C_2} = \frac{(67 \mu\text{C})^2}{2 \times 20 \mu\text{F}} = 112 \mu\text{J}$

Prob. 7

$$R = \frac{\rho l}{A} = \frac{\rho}{V} l^2$$

$$V = Al$$

$$R' = \frac{\rho}{V} l'^2$$

$$\frac{R'}{R} = \frac{l'^2}{l^2} = 100$$

$$R' = 100 R = 1.000 \times 10^4 \Omega$$

Prob. 8

$$R_{eq} = \frac{1.00 \text{ k}\Omega}{10} = 100. \Omega$$

$$I_{eq} = \frac{V}{R_{eq}} = \frac{10.0}{100} = 0.10 \text{ A}$$

$$I = \frac{I_{eq}}{10} = 0.010 \text{ A}$$

Prob. 9

junction b:  $I_3 = I_1 + I_2$

loop fabef:  $V_1 - I_1 R_1 - I_3 R_3 = 0$

loop dcbed:  $V_2 - I_2 R_2 - I_3 R_3 = 0$

$$(R_1 + R_3) I_1 + R_3 I_2 = V_1$$

$$R_3 I_1 + (R_2 + R_3) I_2 = V_2$$

$\Rightarrow$

$$200 I_1 + 100 I_2 = 10$$


$$100 I_1 + 200 I_2 = 20$$

$\Rightarrow$

$$I_1 = 0$$

$$I_2 = 0.10 \text{ A}$$

$$I_3 = 0.10 \text{ A}$$

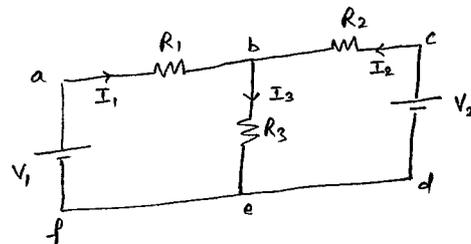

Prob. 10

$$Q(t) = Q_0 e^{-\frac{t}{RC}}$$

$$\frac{1}{2} Q_0 = Q_0 e^{-\frac{t}{RC}}$$

$$\ln \frac{1}{2} = -\frac{t}{RC}$$

$$t = RC \ln 2$$

$$= 1.40 \times 10^{-3} \ln 2$$

$$= 0.693 \times 1.40 \times 10^{-3} \text{ s}$$

$$= 9.70 \times 10^{-4} \text{ s}$$

