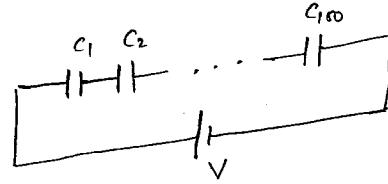


Prob. 1

$$C = \frac{Q}{V} = \frac{20 \mu C}{20.0 V} = 1.00 \mu F.$$


Prob. 2

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_{100}}$$

$$\frac{1}{C_{eq}} = \frac{100}{C}$$

$$C_{eq} = \frac{C}{100}$$

Prob. 3





$$Q_1 = C_1 V_1 = 10.0 \mu F \times 10.0 V = 1.00 \times 10^{-4} C$$

$$Q_2 = C_2 V_2 = 20.0 \mu F \times 10.0 V = 2.00 \times 10^{-4} C$$

$$Q_2 = C_2 V_2 = \frac{(1.00 \times 10^{-4})^2}{2 \times 10.0 \times 10^{-6}} = 0.500 \times 10^{-3} J$$

$$U_1 = \frac{Q_1^2}{2C_1} = \frac{(1.00 \times 10^{-4})^2}{2 \times 10.0 \times 10^{-6}} = 0.500 \times 10^{-3} J$$

$$U_2 = \frac{Q_2^2}{2C_2} = \frac{(2.00 \times 10^{-4})^2}{2 \times 20.0 \times 10^{-6}} = 1.000 \times 10^{-3} J$$

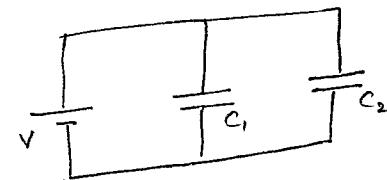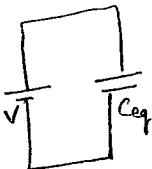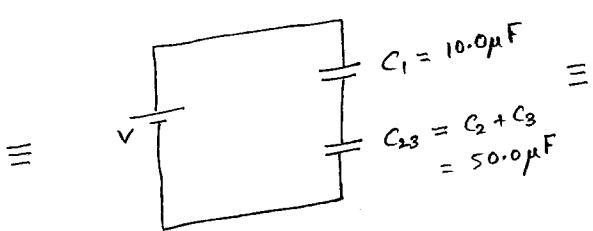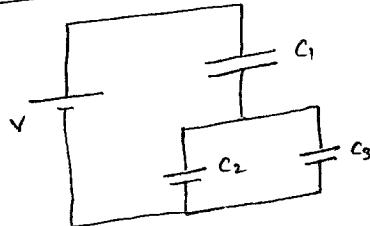
Prob. 4


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_{23}} = \frac{1}{10 \times 5} + \frac{1}{50} = \frac{6}{50} \Rightarrow C_{eq} = \frac{50.0}{6} = 8.33 \mu F$$

$$Q_{eq} = C_{eq} V = 8.33 \mu F \times 10.0 V = 83.3 \mu C$$

$$Q_1 = Q_{eq} = 83.3 \mu C$$

Prob. 5

$$R = \frac{9l}{A}$$

$$R' = \frac{9l'}{A'} = \frac{9 \cdot 3l}{(A/3)} \\ = 9 \cdot \frac{9l}{A} = 9R.$$

$$lA = l'A' \quad (\text{fixed volume})$$

$$= 3l A'$$

$$\Rightarrow A' = \frac{A}{3}$$

Prob. 6

$$I = \frac{P}{V} = \frac{60 \text{ W}}{120 \text{ V}} = 0.50 \text{ A}$$

$$Q = I \times \text{time} = \frac{60}{120} \times 12 \times 60 \times 60 = 2.2 \times 10^4 \text{ C}$$

$$Q = I \times \text{time} = \frac{60}{120} \times 12 \times 60 \times 60 = 2.2 \times 10^4 \text{ C}$$

Prob. 7

$$V = V_1 = V_2 = V_3 = 10.0 \text{ V}$$

$$I_1 = I_2 = I_3 = \frac{V}{R} = \frac{10.0}{300.0} = 33.3 \text{ mA}$$

$$P_1 = P_2 = P_3 = I_1 V_1 = 33.3 \times 10^{-3} \text{ A} \times 10.0 \text{ V}$$

$$= 333 \text{ mW}$$

Prob. 8


$$+V_1 - I_1 R_1 - V_2 = 0$$

$$I_1 = \frac{V_1 - V_2}{R_1} = \frac{10.0 - 2.00}{100.0}$$

$$= -0.100 \text{ A}$$

$$= -100 \text{ mA}$$


Direction of I_1 is opposite to that shown in figure.

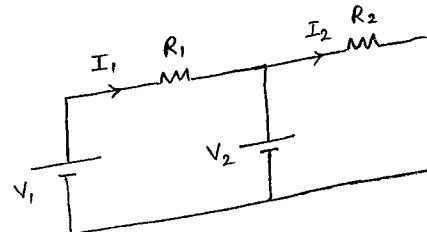

Prob. 9

$$V_1 - I_1 R_1 - I_3 R_3 = 0 \Rightarrow I_1(R_1 + R_3) + I_2 R_3 = V_1$$
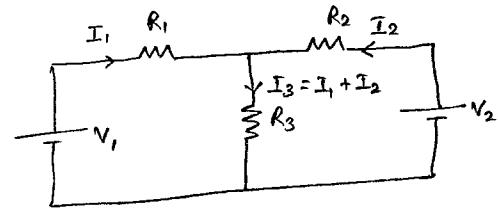
$$V_2 - I_2 R_2 - I_3 R_3 = 0 \Rightarrow I_1 R_3 + I_2(R_2 + R_3) = V_2.$$



$$40 I_1 + 30 I_2 = 10$$

$$30 I_1 + 40 I_2 = 20$$

$$I_1 = \frac{10 \times 40 - 20 \times 30}{40 \times 40 - 30 \times 30} = \frac{4-6}{16-9} = -\frac{2}{7}$$

$$I_2 = \frac{40 \times 20 - 30 \times 10}{40 \times 40 - 30 \times 30} = \frac{8-3}{16-9} = +\frac{5}{7}$$

$$I_3 = I_1 + I_2 = -\frac{2}{7} + \frac{5}{7} = +\frac{3}{7} = 0.429 \text{ A}$$

(direction is the same as shown in figure.)

Prob. 10

$$(a) V - IR - \frac{Q}{C} = 0$$

$$(b) Q(t) = CV \left[1 - e^{-\frac{t}{RC}} \right]$$

$$\begin{aligned} Q_{\max} &= CV \\ &= 10.0 \mu F \times 10.0 \text{ V} \\ &= 1.00 \times 10^{-4} \text{ C} \end{aligned}$$

It takes infinite time to charge the capacitor to this value.

