

Midterm Exam 02 (2016 Fall)

PHYS 203B: College Physics

Date: 2015 Oct 13

(Name)

(Signature)

Instructions

1. Seating direction: Please be seated on seats with seat-numbers divisible by 3.
2. Total time = 75 minutes.
3. There are 9 questions in this exam.
4. Equation sheet is provided separately.
5. To be considered for partial credit you need to show your work in detail and organize it clearly.
6. A simple calculator (with trigonometric functions) is allowed.
7. Use of mobile phones is strictly prohibited. It should stay out of reach during the exam.

1. **(10 points.)** The average cost of energy delivered to residences by electrical transmission in Illinois is 0.12 USD per kWh. At this price, calculate the cost of leaving a 100.0 W porch light on for two weeks while you are on vacation.

2. **(10 points.)** Two identical capacitors store different amounts of energy: capacitor A stores 8.0×10^{-3} J, and capacitor B stores 2.0×10^{-3} J. The charge stored in capacitor B is $1.0 \mu\text{C}$. Find the charge stored in capacitor A.

3. (10 points.) A potential difference $V = 10.0\text{ V}$ is applied across a capacitor arrangement with two capacitances connected in parallel, $C_1 = 10.0\text{ nF}$ and $C_2 = 20.0\text{ nF}$.

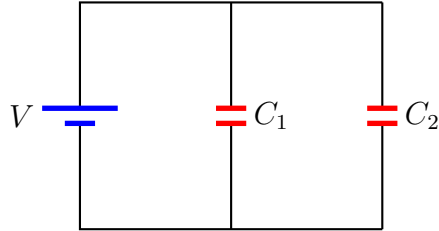


Figure 1: Problem 3

- (a) Find the equivalent capacitance.
- (b) Find the ratio V_1/V_2 of the voltages across the capacitors.
- (c) Find the ratio Q_1/Q_2 of the charges on the capacitors.
- (d) Find the ratio U_1/U_2 of the potential energies stored inside the capacitors.

4. (**10 points.**) Figure 2 shows three resistors connected in parallel to a battery. The battery has a voltage of $V = 10.0\text{ V}$, and the resistors have equal resistances of $R = 300.0\ \Omega$.
- (a) Determine the equivalent resistance across the battery.
 - (b) Determine the voltage across each of the resistor.
 - (c) Determine the current passing through each resistor.
 - (d) Determine the power consumed by each resistor.

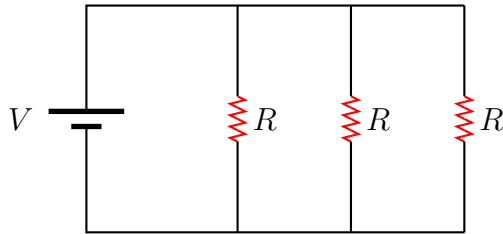


Figure 2: Problem 4

5. (10 points.) In Figure 3 determine the equivalent resistance between points a and b . Let $R = 7.00\ \Omega$.

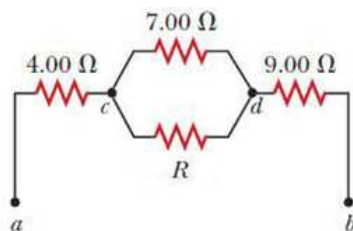


Figure 3: Problem 5.

6. (10 points.) In the circuit in Figure 4 determine the charge on capacitor C_1 . Let $V = 10.0\text{ V}$, $C_1 = 10.0\text{ nF}$, $C_2 = 20.0\text{ nF}$, and $C_3 = 30.0\text{ nF}$.

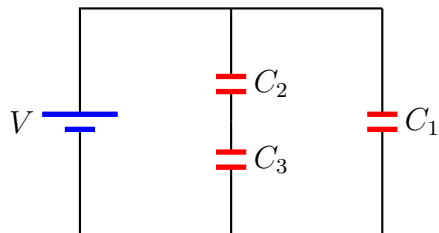


Figure 4: Problem 6.

7. **(10 points.)** A parallel-plate capacitor has an area of 5.10 cm^2 , and the plates are separated by 4.4 mm . The capacitor stores a charge of 400.0 pC . What is the potential difference across the plates of the capacitor?

8. **(10 points.)** The resistance R of a wire of length l and uniform area of cross-section A is given by

$$R = \frac{\rho l}{A}, \quad (1)$$

where ρ is the resistivity of the wire. You melt the wire and recast it to have a new length $l' = 10l$ (keeping the volume $V = Al$ of the wire constant). What is the new resistance of the wire, if the original resistance of the wire was $100.0\,\Omega$.