

# Midterm Exam 02 (2017 Spring)

## PHYS 203B-001: College Physics

Date: 2017 Mar 10

---

(Name)

---

(Signature)

### Instructions

1. Seating direction: Please be seated on seats with seat-numbers divisible by 3.
2. Total time = 50 minutes.
3. There are 8 questions in this exam.
4. Equation sheet is provided separately.
5. To be considered for partial credit you need to show your work in detail and organize it clearly.
6. A simple calculator (with trigonometric functions) is allowed.
7. Use of mobile phones is strictly prohibited. It should stay out of reach during the exam.

1. (**10 points.**) The average cost of electricity in the United States, for residential users, is about 0.12 USD/kWh (12 cents per kilo-Watt-hour). At this rate your electricity bill for a month came out to be 50.00 USD. How much electric energy (in Joules) did you use in the month?

2. **(10 points.)** A piece of Nichrome wire of resistivity  $1.50 \times 10^{-6} \Omega\text{m}$  has a radius of  $6.50 \times 10^{-4} \text{m}$  and a total length of 15 m. It is used in a laboratory to make a heater when connected to a voltage source of 120 V. Ignoring the effect of temperature on resistance, estimate the power output of the heater.

3. (10 points.) Determine the equivalent capacitance between points  $A$  and  $B$  in the circuit in Figure 1. Given  $C_1 = 1.0\ \mu\text{F}$ ,  $C_2 = 2.0\ \mu\text{F}$ ,  $C_3 = 3.0\ \mu\text{F}$ , and  $C_4 = 4.0\ \mu\text{F}$ .

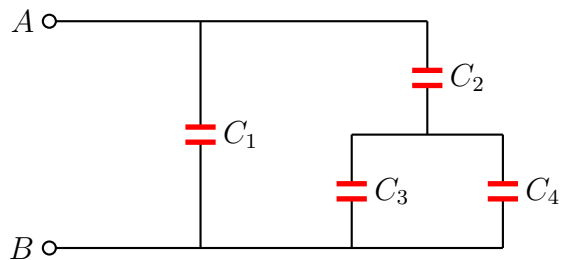


Figure 1: Problem 3

4. (10 points.) Figure 2 shows two resistors connected in parallel to a battery. The battery has a voltage of  $V = 10.0\text{ V}$ , and the resistors have resistances  $R_1 = 100.0\,\Omega$  and  $R_2 = 200.0\,\Omega$ .

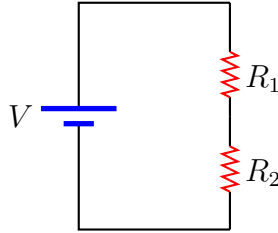


Figure 2: Problem 4

- (a) Find the ratio  $P_1/P_2$  of the powers of the resistors.
- (b) If the resistors represented electric bulbs, which bulb would glow brighter?

5. (10 points.) A potential difference  $V = 10.0\text{ V}$  is applied across a capacitor arrangement with two capacitances connected in series,  $C_1 = 10.0\text{ }\mu\text{F}$  and  $C_2 = 20.0\text{ }\mu\text{F}$ .

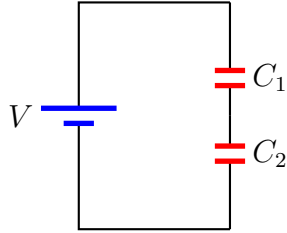


Figure 3: Problem 5

- (a) Find the equivalent capacitance.
- (b) Find the charges  $Q_1$  and  $Q_2$  on each of the capacitors.
- (c) Find the voltages  $V_1$  and  $V_2$  across each of the capacitors.
- (d) Find the potential energies  $U_1$  and  $U_2$  stored inside each of the capacitors.

6. (10 points.) A charge particle enters a uniform magnetic field and follows the path shown in Fig. 4. What can you conclude about the charge of the particle, that is, is it positive, negative, or neutral?

Advice: Write a few lines elaborating on the method you used to arrive at the solution. This will help you earn partial credit, if necessary.

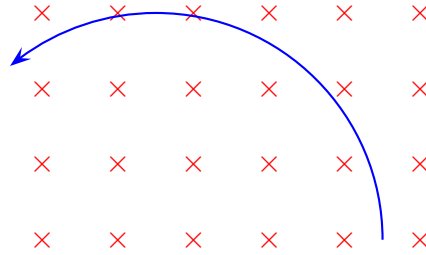


Figure 4: Problem 6

7. **(10 points.)** An electron, is traveling at a velocity of  $5.1 \times 10^6$  m/s due East, in a magnetic field that has a magnitude of 0.10 Tesla along a direction  $30^\circ$  West of North. (Caution: Be careful while interpreting the angle.)
- (a) What is the magnitude of the magnetic force acting on the electron?
  - (b) What is the direction of the magnetic force acting on the electron? (Use the notation,  $+x$  for East,  $-x$  for West,  $+y$  for North,  $-y$  for South,  $+z$  for vertically up, and  $-z$  for vertically down.)

8. (10 points.) A loop in the shape of a right triangle, carrying a current  $I = 2.0\text{ A}$ , is placed in a magnetic field  $B = 2.0\text{ T}$ . (Choose  $\hat{\mathbf{z}}$  to be out of the page, and  $\hat{\mathbf{x}}$  to be along side 1 of the triangle.) Let  $x = 3.0\text{ cm}$ ,  $y = 2.0\text{ cm}$ .

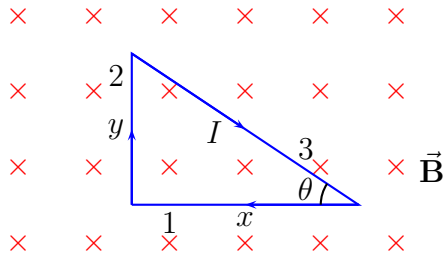


Figure 5: Problem 8.

- Determine the magnitude and direction of the magnetic force on side 1 of the triangle.
- Determine the magnitude and direction of the magnetic force on side 2 of the triangle.