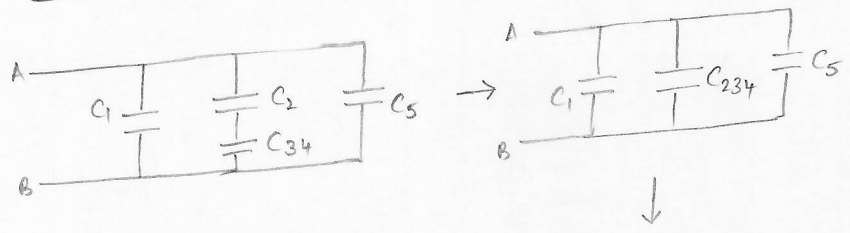


Solutions

Problem 1



$$C_{eq} = C_1 + C_{234} + C_5$$

$$= 1.0 + \frac{14}{9.0} + 5.0$$

$C_{eq} = 7.6 \mu F$ → Answer.

$$C_{34} = C_3 + C_4$$

$$= 3.0 + 4.0 = 7.0 \mu F$$

$$\frac{1}{C_{234}} = \frac{1}{C_2} + \frac{1}{C_{34}}$$

$$= \frac{1}{2.0} + \frac{1}{7.0} = \frac{9.0}{14}$$

$$C_{234} = \frac{14}{9.0} \mu F$$

Problem 2


loop rule (rectangle): $+V - IR = 0$

$$\Rightarrow I = \frac{V}{R}$$

loop rule for abca:

$$+V - IR = 0$$

$$\Rightarrow I = \frac{V}{R}$$

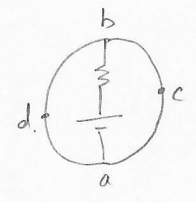

Thus, current is same in both cases.

Problem 3

$$\left. \begin{aligned} V &= IR \\ V &= \frac{Q}{C} \end{aligned} \right\} \Rightarrow [RC] = \frac{[Q]}{[I]} = \text{Time} = T$$

Problem 4

$$\omega = \frac{qB}{m} = \frac{(1.6 \times 10^{-19})(0.50 \times 10^4)}{(9.1 \times 10^{-31})}$$


$$= 8.8 \times 10^6 \text{ Hz}$$

$$R = \frac{v}{\omega} = \frac{1.0 \times 10^7}{8.8 \times 10^6}$$

$$= 1.1 \text{ meter}$$

$R < 1.1$ meter depending on direction of initial velocity.

Problem 5

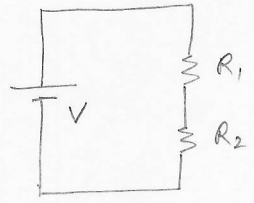

(a) $R_{eq} = R_1 + R_2$
 $= 100.0 + 200.0 = 300.0 \Omega$


(b) $I_1 = I_2 = \frac{V}{R_{eq}} = \frac{10.0}{300.0} = 33.3 \text{ mA}$

(c) $V_1 = I_1 R_1 = (33.3 \times 10^{-3})(100.0) = 3.33 \text{ Volts}$
 $V_2 = I_2 R_2 = (33.3 \times 10^{-3})(200.0) = 6.66 \text{ Volts}$

(d) $P_1 = I_1^2 R_1 = (33.3 \times 10^{-3})^2 (100.0) = 0.111 \text{ Watts}$
 $P_2 = I_2^2 R_2 = (33.3 \times 10^{-3})^2 (200.0) = 0.222 \text{ Watts}$

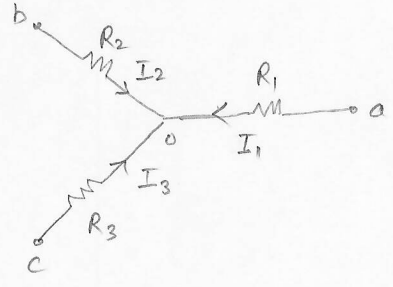Problem 6

junction rule at 0: $I_1 + I_2 + I_3 = 0$
 $\Rightarrow I_3 = -I_1 - I_2$



Path coa: $+V_c - I_3 R_3 + I_1 R_1 = V_a$
 $30.0 - (-I_1 - I_2) 30.0 + I_1 (10.0) = +10.0$
 $40.0 I_1 + 30.0 I_2 = -20.0 \quad \text{--- (1)}$

Path boa: $+V_b - I_2 R_2 + I_1 R_1 = V_a$
 $20.0 - I_2 20.0 + I_1 10.0 = 10.0$
 $10.0 I_1 - 20.0 I_2 = -10.0 \quad \text{--- (2)}$

Using (1) & (2)

$I_1 = \frac{\begin{vmatrix} -20.0 & 30.0 \\ -10.0 & -20.0 \end{vmatrix}}{\begin{vmatrix} 40.0 & 30.0 \\ 10.0 & -20.0 \end{vmatrix}} = \frac{+400. + 300.}{-800. - 300.} = -0.636 \text{ A}$
 $I_2 = \frac{\begin{vmatrix} 40.0 & -20.0 \\ 10.0 & -10.0 \end{vmatrix}}{\begin{vmatrix} 40.0 & 30.0 \\ 10.0 & -20.0 \end{vmatrix}} = \frac{-400. + 200.}{-800. - 300.} = +0.182 \text{ A}$

$I_3 = -I_1 - I_2$
 $= +0.455 \text{ A}$

Problem 7

Total force on the loop is zero (in uniform \vec{B})

Thus,

$$\vec{F}_{atb} + \vec{F}_{boa} = 0$$

$$\vec{F}_{atb} = -\vec{F}_{boa}$$

$$= -I L_{boa} \underbrace{\hat{x} \times \hat{x}}_{=0} \cdot \vec{B}$$

$$= 0$$

Segment atb experiences no force.

